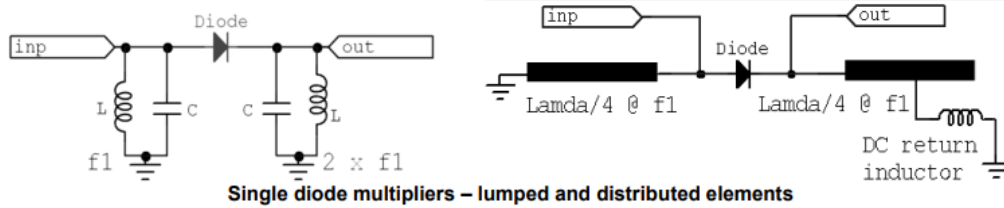


Configuration 1

<https://docs.amprntrs.ru/eevblog.docs/ Materials/Frequency multiplier circuits survey and theory ROSU.pdf>


The additional diode results in the suppression of even order products, the enhancement of odd order products, and the elimination of the bias resistor.




The stub at the left is a quarter-wave transformer. It transforms the short to open and decreases the f_0 reflecting from the diode.

The stub at the right is a quarter-wave transformer. It transforms the open to short and sends f_0 signals to ground to enhance the dominance of the second harmonic.


Simulation of Lumped Configuration

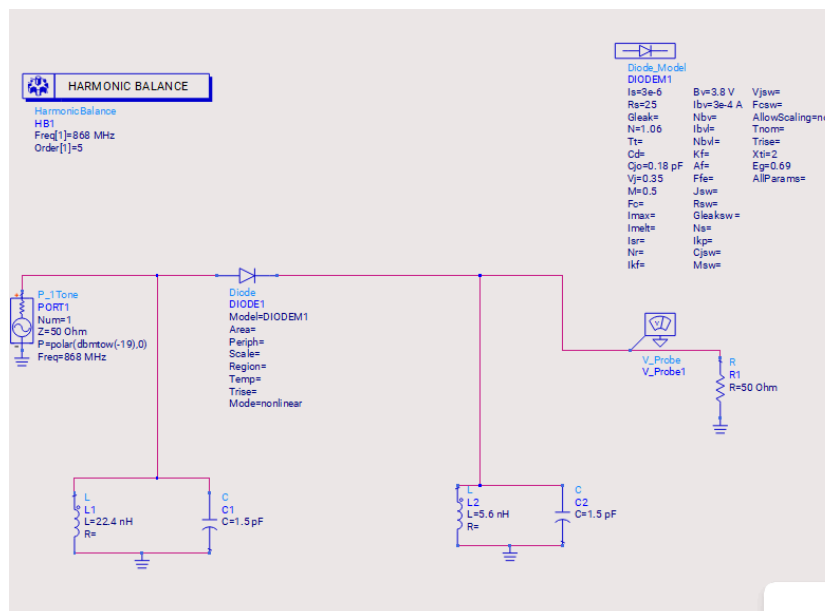

m1	m2	m3
freq=868.0 MHz	freq=1.736 GHz	freq=2.604 GHz
dBm(net)=-42.922	dBm(net)=-57.650	dBm(net)=-69.749


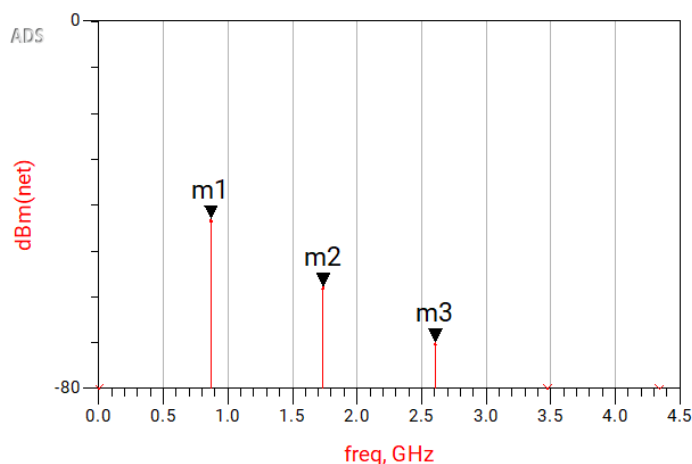


Simulation of Distributed Configuration

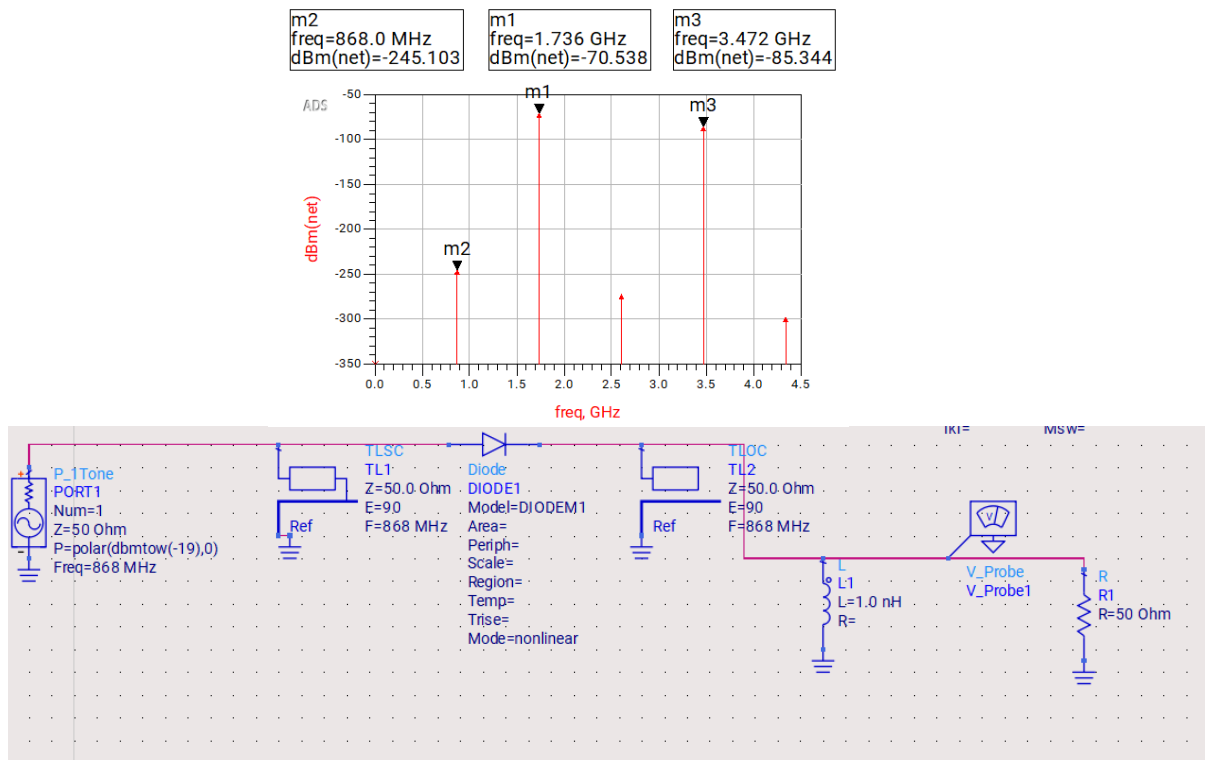



Configuration 2

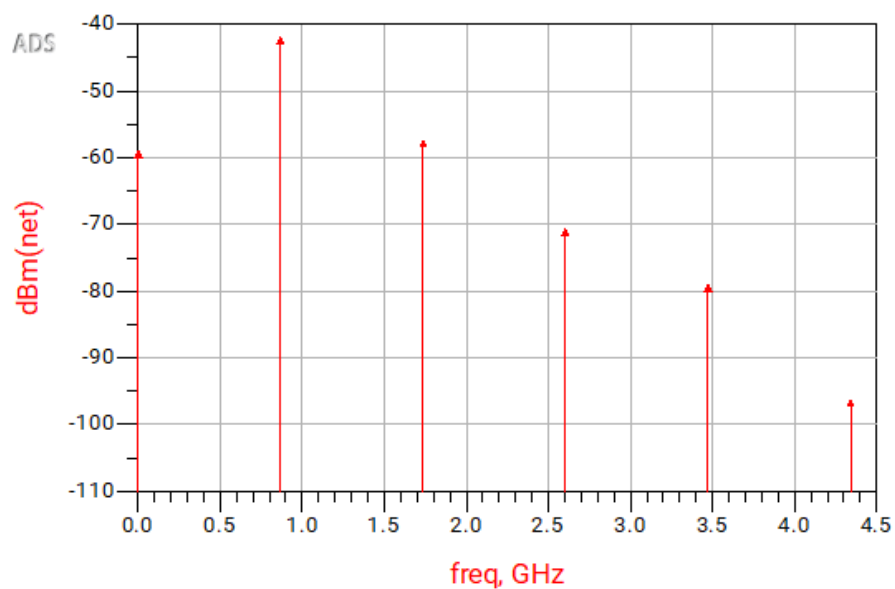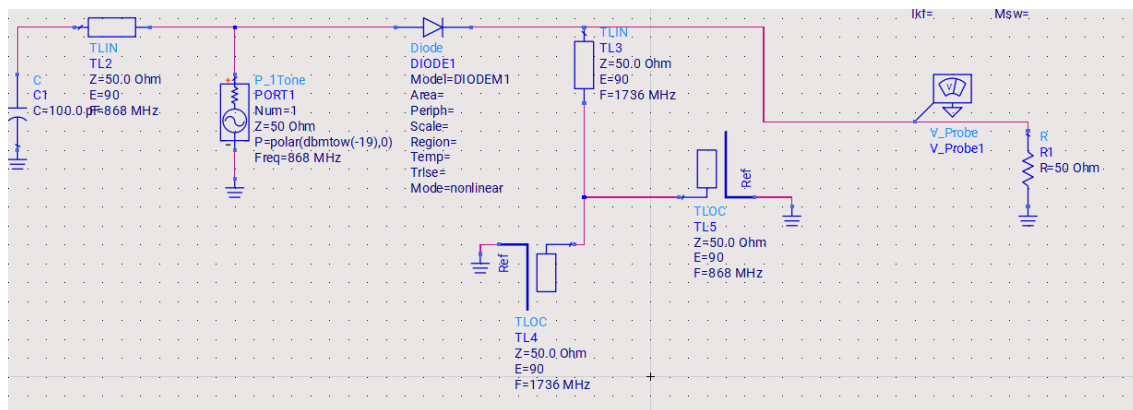This is the exact configuration of the frequency doubler described in Figure 2 in the article.



Configuration 3

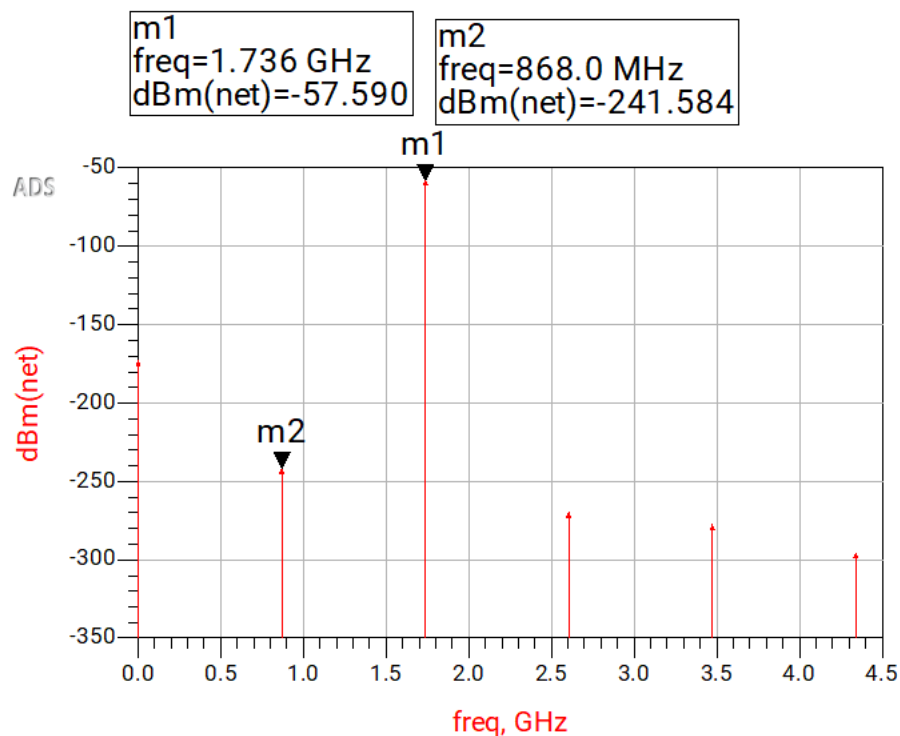
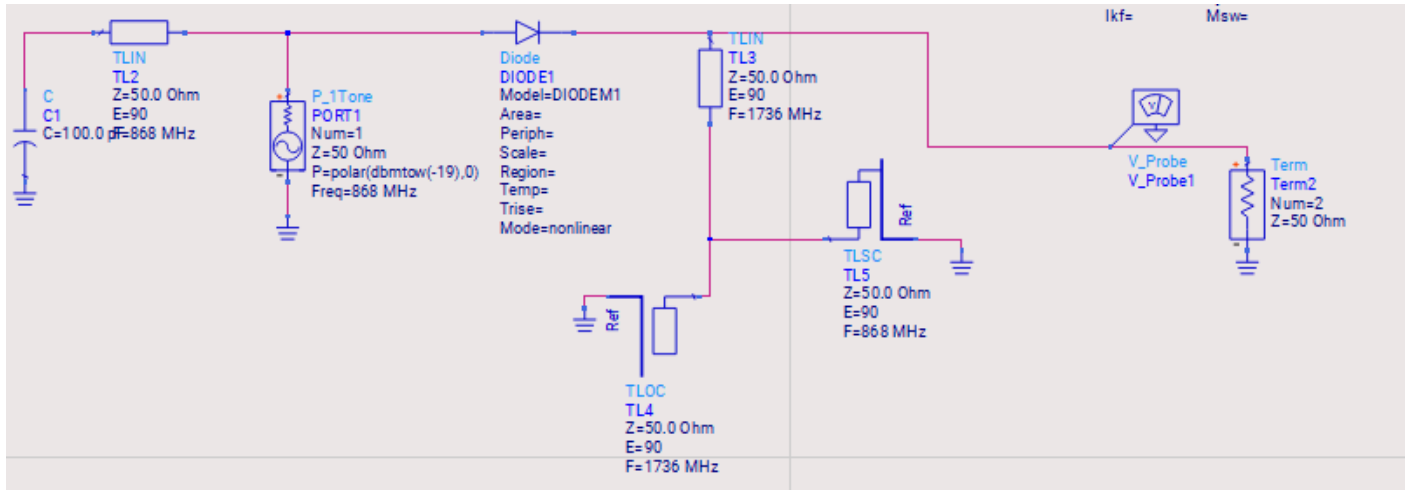
There is a ambiguity about the one of the stubs in article. In the article, in Figure 3 stub is connected to ground whereas in Figure 2 it is indicated at it is left open. When I change Configuration 2 by connecting that ambiguous stub to ground, output changes.




It can be observed that 2nd harmonic is very dominant among all harmonics that occur at the output.

Configuration 4

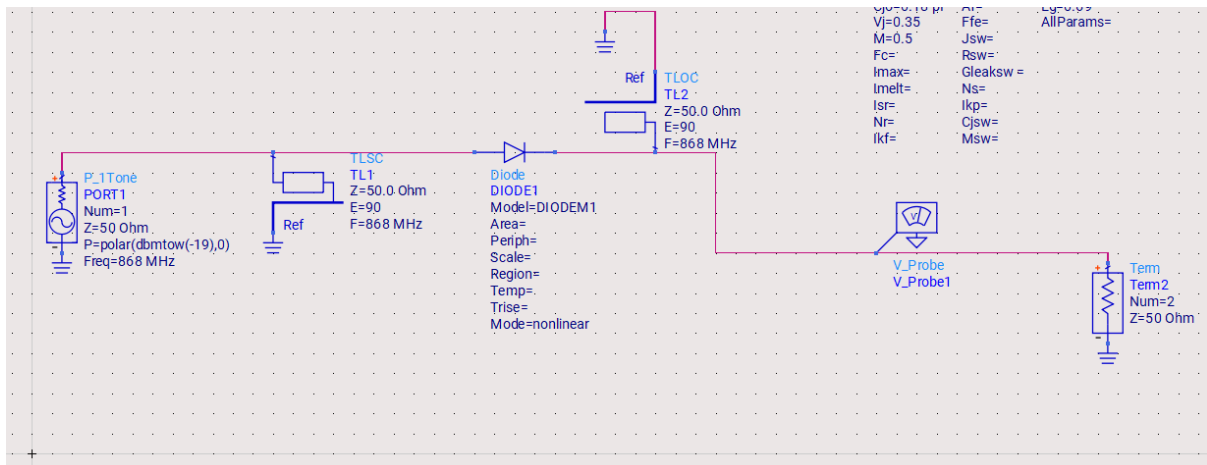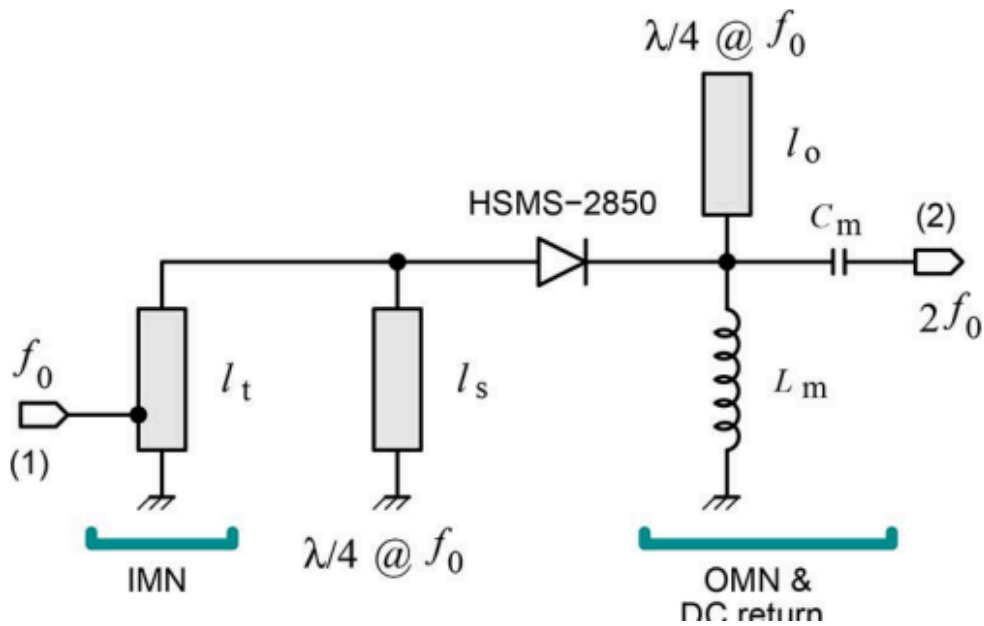https://www.researchgate.net/publication/273396192_Low-Power_Frequency_Doubler_in_Cellulose-Based_Materials_for_Harmonic_RFID_Applications



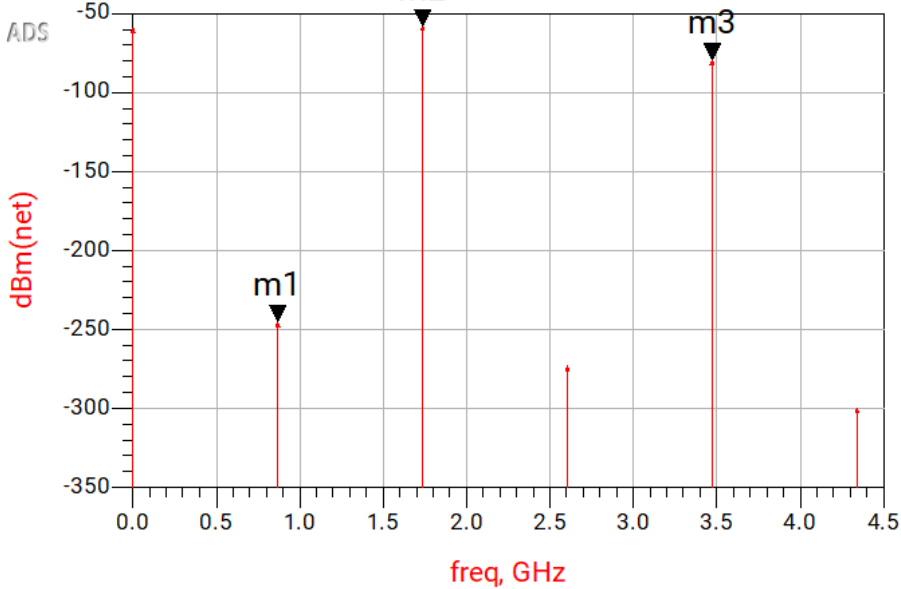

Configuration 5

https://www.researchgate.net/publication/224302687_A_single-diode_frequency_doubler_using_a_feed-forward_technique


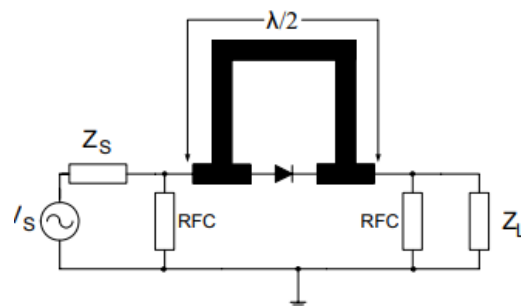


Fig. 1. Simplified feed-forward microstrip design

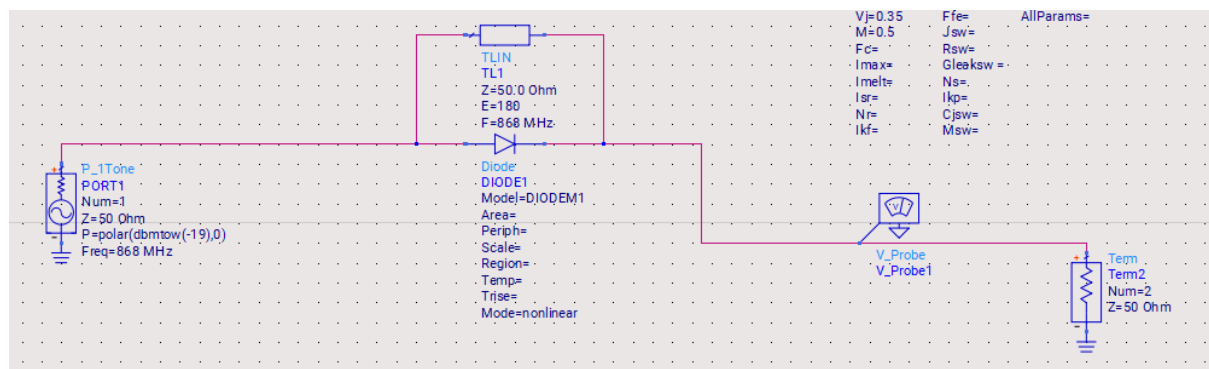

m1
freq=868.0 MHz
dBm(net)=-19.248

m2
freq=1.736 GHz
dBm(net)=-386.339

